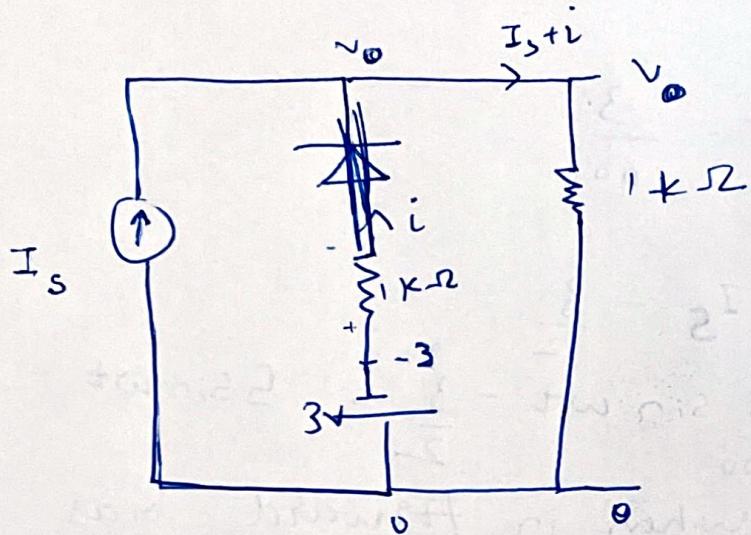


Q1) Case 1:- D in forward bias :-



$$i > 0$$

$$V_o < -3$$

$$V_o = (I_s + i) \cdot 1000$$

$$i = \frac{-3 - V_o}{1000}$$

$$\left[ I_s - \frac{(V_o + 3)}{1000} \right] \cdot 1000 < -3$$

$$I_s - \frac{V_o}{1000} - \cancel{\frac{3}{1000}} < \cancel{\frac{-3}{1000}}$$

$$I_s < \frac{V_o}{1000}$$

$$I_s < -\cancel{\frac{3}{1000}}$$

So for  $10 \sin \omega t < -3$ , diode is forward bias &  $10 \sin \omega t > -3$ , diode is reverse bias.

$$\frac{V_o}{1000} = I_S - \frac{V_o + 3}{1000}$$


$$\frac{2V_o}{1000} = I_S - \frac{3}{1000}$$

$$V_o = 5000 I_S - \frac{3}{2}$$

$$V_o = \frac{5000 \sin \omega t - 3}{1000} = 5 \sin \omega t - \frac{3}{2}$$



when in forward bias

case 2:-  $\Delta$  in reverse bias

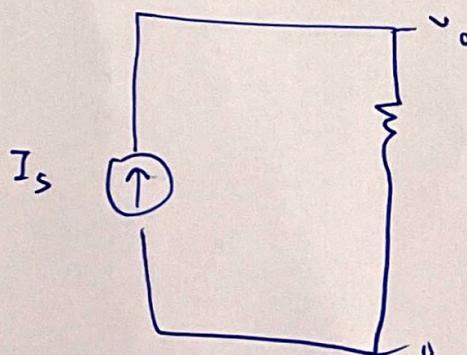

$$\begin{aligned} V_o &= 1000 I_S \\ &= \frac{10000 \sin \omega t}{1000} \\ &= 10 \sin \omega t \end{aligned}$$
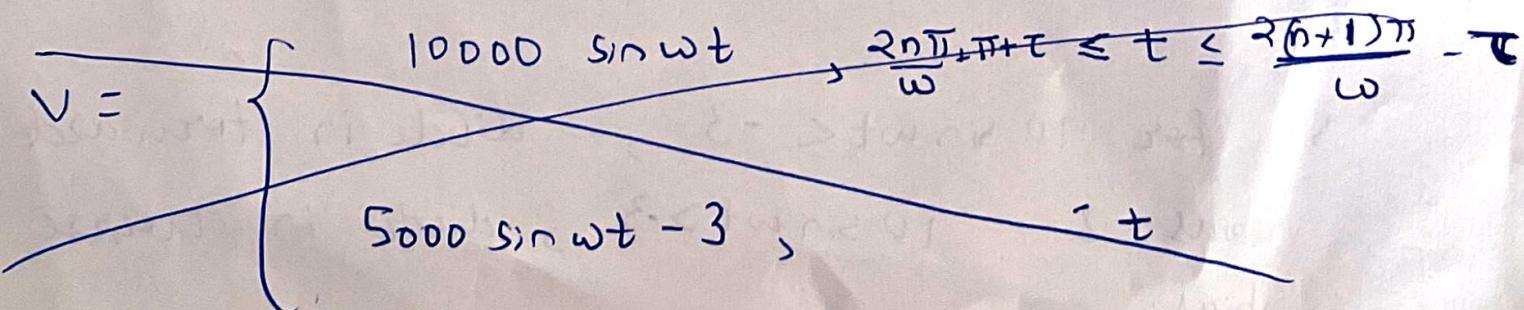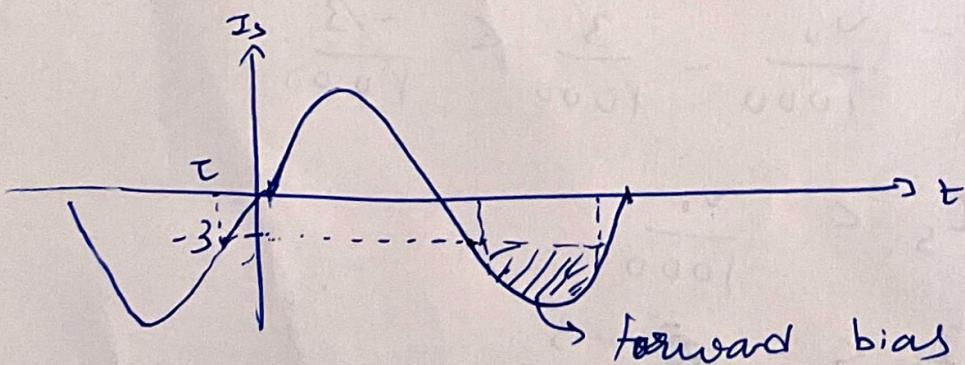
$$\text{Let } \tau = \frac{1}{\omega} \sin^{-1} \frac{-3}{10} = -\frac{1}{\omega} \sin^{-1} \frac{3}{10}$$



$$v = \begin{cases} 10 \sin \omega t & 0 \leq t \leq \frac{(n+1)\pi}{\omega} + \tau \\ 5 \sin \omega t - \frac{3}{2} & \frac{(n+1)\pi}{\omega} + \tau \leq t \leq \frac{(n+2)\pi}{\omega} - \tau \end{cases}$$

(Q2)

$$\begin{aligned} \frac{v_r}{v_i} &= \frac{R \parallel X_L}{Z} \\ &= \frac{\frac{R \cdot \omega L i}{R + \omega L i}}{\frac{R \cdot \omega L i}{R + \omega L i} + -\frac{i}{\omega C}} \\ &= \cancel{\frac{R \omega L}{R + \omega L i}} \\ &= \frac{\frac{R \omega L}{R + \omega L i} - \frac{1}{\omega C}}{\frac{R \omega^2 L C}{R \omega^2 L C - R - \omega L i}} \\ &= \frac{R \omega^2 L C}{R [ \omega^2 L C - 1 ] - \omega L i} \end{aligned}$$

$$H(\omega) = \frac{R^2 \omega^2 LC [\omega^2 LC - 1] + R\omega^3 L^2 C i}{R^2 [\omega^2 LC - 1]^2 + \omega^2 L^2}$$

$$\operatorname{Re}(H(\omega)) = \frac{R^2 LC \omega^2 [\omega^2 LC - 1]}{R^2 [\omega^2 LC - 1]^2 + \omega^2 L^2}$$

For  $\operatorname{Re}(H(\omega)) = 0$ ,

$$\omega^2 [\omega^2 LC - 1] = 0$$

$\omega = 0 \quad \text{or} \quad \frac{1}{\sqrt{LC}}$

$$\begin{aligned}
 H(\omega) &= \frac{R^2 \omega^3 LC [\omega^2 LC - 1] + R\omega^3 L^2 C i}{\omega^2 L^2 \left[ R^2 \left[ \frac{\omega^2 LC - 1}{\omega L} \right]^2 + 1 \right]} \\
 &= \frac{R^2 \omega^2 LC [\omega^2 LC - 1] + R\omega^3 L^2 C i}{\omega^2 L^2 \left[ R^2 \left[ \omega C - \frac{1}{\omega L} \right]^2 + 1 \right]} \\
 &\approx \frac{R^2 \frac{C}{L} [\omega^2 LC - 1] + R\omega C i}{R^2 \left[ \omega C - \frac{1}{\omega L} \right]^2 + 1}
 \end{aligned}$$

$$H(\omega) = \frac{R^2 \frac{C}{L} [\omega^2 LC - 1] + R\omega C i}{-2R^2 \frac{C}{L} + R^2 \omega^2 L^2 + \frac{R^2}{\omega^2 L^2} + 1}$$

$$\approx \frac{R^2 \frac{C}{L} [\omega^2 LC - 1] + R\omega C i}{R^2 \left[ \omega C - \frac{1}{\omega L} \right]^2}$$


[  $\therefore 1$  negligible compared  
 $\omega - 2R^2 \frac{C}{L}$  ]

~~$$H(\omega) = \omega R^2 \frac{C^2}{L} \left[ \omega C - \frac{1}{\omega L} \right] + R i$$~~


$$H(\omega) = \frac{R^2 \omega C \left[ \omega C - \frac{1}{\omega L} \right] + R\omega C i}{R^2 \left[ \omega C - \frac{1}{\omega L} \right]^2}$$

$$\operatorname{Re}(n) = \frac{\omega C}{\omega C - \frac{1}{\omega L}}$$
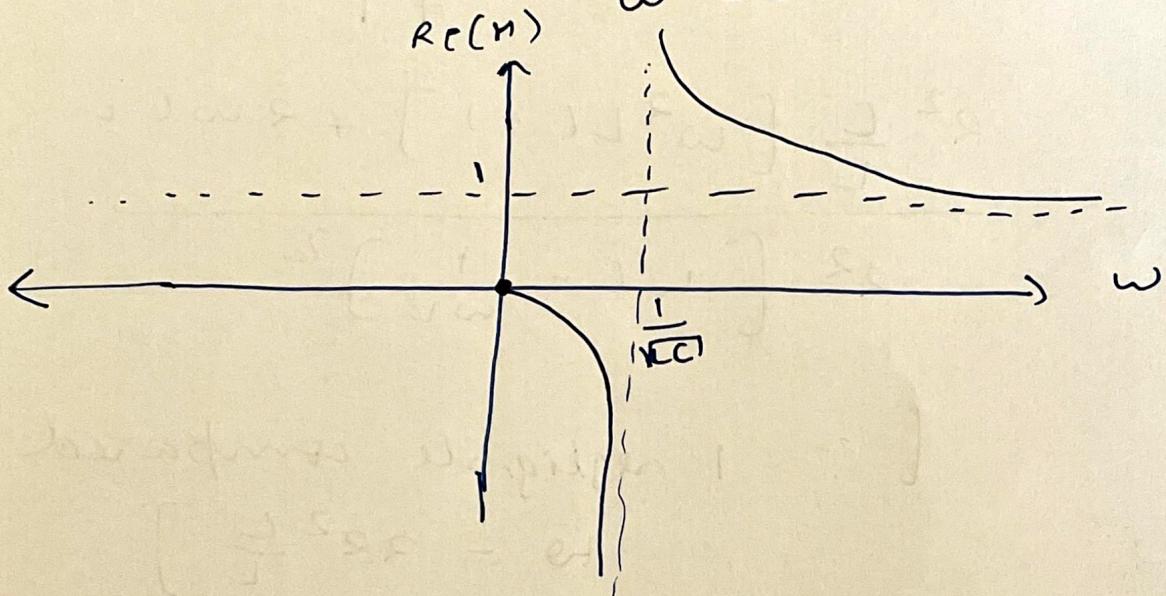
$$= \frac{\omega^2 LC}{\omega^2 LC - 1}$$


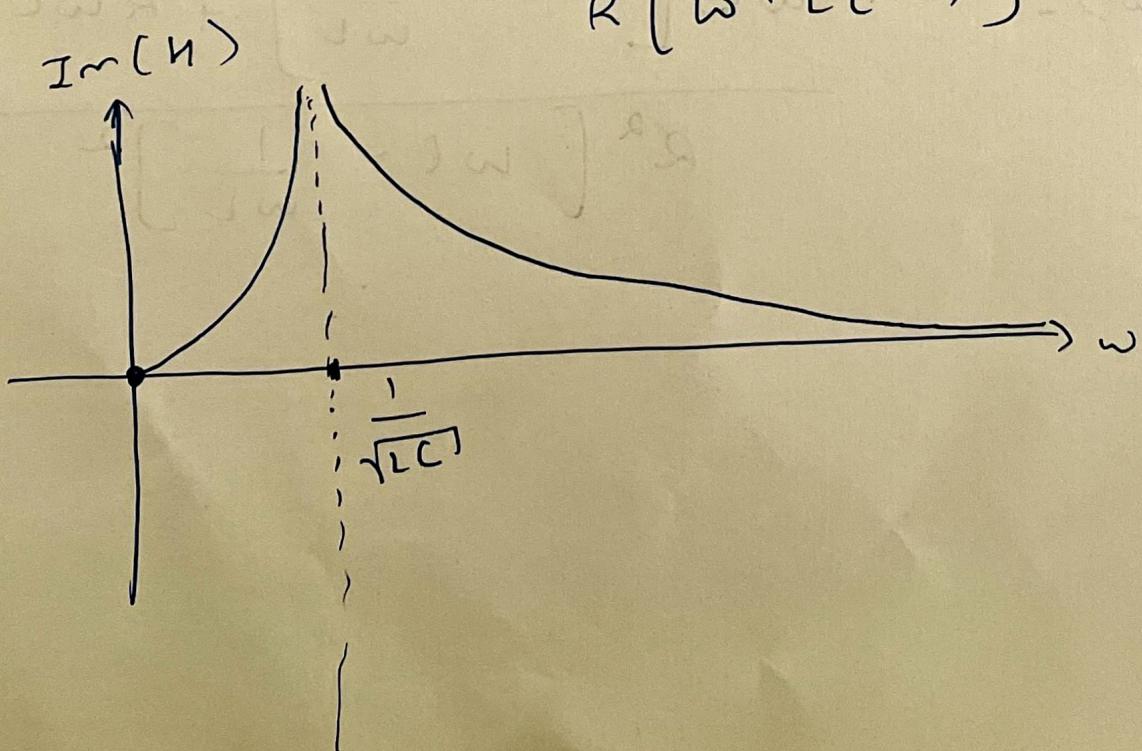
$$\begin{aligned} \operatorname{Im}(n) &= \frac{\omega C}{R \left[ \omega C - \frac{1}{\omega L} \right]^2} \\ &= \frac{\omega^3 L^2 C}{R \left[ \omega^2 L C - 1 \right]^2} \end{aligned}$$



$$abs(H) = \frac{R \omega C \sqrt{R^2 \left( \omega C - \frac{1}{\omega L} \right)^2 + 1}}{R^2 \left[ \omega C - \frac{1}{\omega L} \right]^2}$$

$$\approx \frac{R \omega C \cdot R \left( \omega C - \frac{1}{\omega L} \right)}{R^2 \left[ \omega C - \frac{1}{\omega L} \right]^2}$$


$\therefore [R^2 \cancel{\frac{1}{\omega L}} \gg 1]$

$$= \frac{\omega C}{\omega C - \cancel{\frac{1}{\omega L}}}$$

$$= \frac{\omega^2 C L}{\omega^2 C L - 1}$$

$$\text{Max}(abs(H)) \rightarrow \infty \quad \text{as } \omega \rightarrow \frac{1}{\sqrt{LC}}$$

(g3)

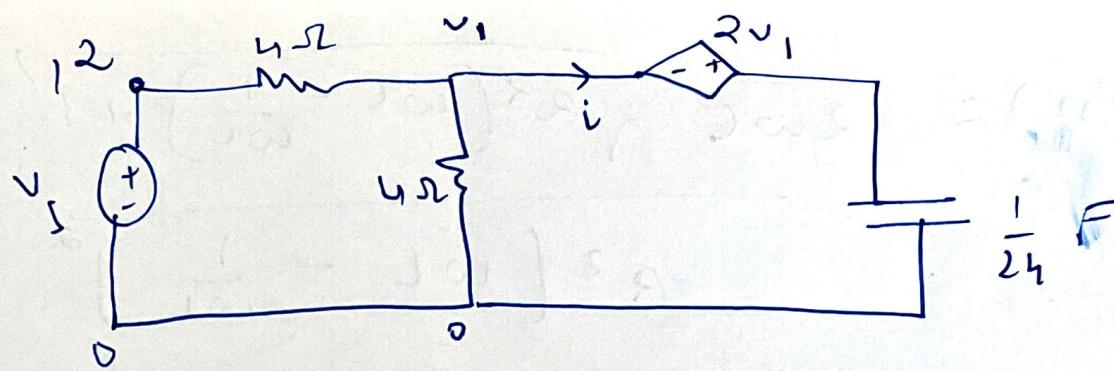

For  $t < 0$ ,

$$v(t) = 0, \quad i(t) = 0$$

For  $t > 0$ ,

$q$  = charge on capacitor

$$\frac{q}{C} = 3v_1 = 3i_1 R_1$$

$$\frac{12 - v_1}{4} = \frac{v_1}{4} + i$$

$$i + i_1 = 3 - i_1$$

$$\dot{i} = 3 - 2i_1 \quad (\text{using } i = \dot{q})$$

$$i_1 = \frac{q}{3R_1 C} = \frac{q}{3 \cdot 4 \cdot \frac{1}{24}} \\ i_1 = 2q$$

$$\frac{dq}{dt} + 4q = 3$$

$$\frac{d}{dt} [e^{4t} \cdot q] = 3e^{4t}$$

$$\cancel{q_r e^{4t}} = \frac{3}{4} e^{4t}$$

$$q_r e^{4t} = \frac{3}{4} e^{4t} + C$$

$$\text{At } t=0, q_r = 0$$

$$0 = \frac{3}{4} + C, C = -\frac{3}{4}$$

$$\therefore q_r = \frac{3}{4} [1 - e^{-4t}]$$

$$\therefore i = -\frac{3}{4} e^{-4t} (-4)$$


$$i = 3 e^{-4t}$$

$$\therefore i(t) = \begin{cases} 0 & t < 0 \\ 3 e^{-4t} & t \geq 0 \end{cases}$$

$$v = \frac{q_r}{C} = 24 q_r \\ = 18 [1 - e^{-4t}]$$

$$v(t) = \begin{cases} 0 & t < 0 \\ 18 [1 - e^{-4t}] & t \geq 0 \end{cases}$$

84)

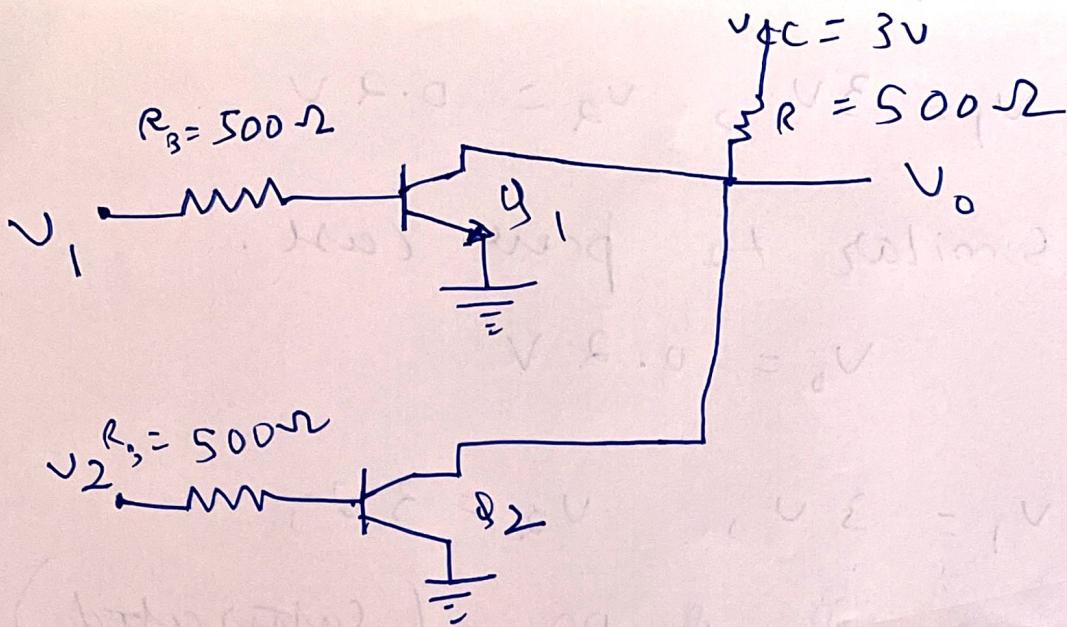

$$\text{If } V_1 = V_2 = 0.2 \text{ V}$$

If Q<sub>1</sub>, Q<sub>2</sub> off,

$$V_o = 3 \text{ V}$$

$$\text{If } V_1 = 0.2 \text{ V}, V_2 = 3 \text{ V}$$

Assume Q<sub>1</sub> off Q<sub>2</sub> on (saturated)

$$V_o = 0.2 \text{ V}$$

$$i_{B_2} = \frac{3 - 0.2}{500} = 4.4 \text{ mA}$$

$$i_{E_2} = \frac{3 - 0.2}{500} = 5.6 \text{ mA}$$

$$\frac{i_{E_2}}{i_{B_2}} = \frac{4.4}{5.6} = 1.27 < \beta$$

Assumption correct.

start again

$$\text{If } V_1 = 3V, \quad V_2 = 0.2V$$

Similar to prev. case.

$$V_o = 0.2V$$

$$\text{If } V_1 = 3V, \quad V_2 = 3V$$

Assume  $\beta_1, \beta_2$  or (saturated)

$$V_o = V_{E_1} = V_{E_2} = 0.2V$$

$$i_{E_1} = i_{E_2} = \frac{1}{2} \cdot \frac{3 - 0.2}{500} = 2.8mA$$

$$i_{B_1} = i_{B_2} = 4.4mA$$

$$\frac{i_{E_1}}{i_{B_1}} = \frac{i_{E_2}}{i_{B_2}} = 0.67 < \beta$$

Assumption correct.

$V_1$	$V_2$	$V_o$
0	0	1
0	1	0
1	0	0
1	1	0

(NOR Gate)


$$\begin{array}{ccccccccc}
 1 & | & 2 & | & 3 & | & 4 & | & 5 & | & 6 & | & 7 & | & 8 \\
 & & & & & & & & & & & & & & \\
 0.2 & & 3 & & 0.2 & & 3 & & 0.2 & & 3 & & - & & \\
 0.2 & & 3 & & 0.2 & & 3 & & 0.2 & & 3 & & - & & \\
 = 3 & & = 0.2 & & = 3 & & = 0.2 & & = 3 & & = 3 & & - & & 
 \end{array}$$

$$\begin{array}{ccc}
 9 & , 0 & \text{original} \\
 | & | & | \\
 & 3 & 0.2 \\
 & 3 & 0.2 \\
 = & \boxed{0.2} & = \boxed{3}
 \end{array}$$

$\therefore$  The output voltage of the gate  
 is ~~0~~ 3 V.

$1 \rightarrow 3$   
 $2 \rightarrow 5$   
 $3 \rightarrow 2$   
 $4 \rightarrow 3$   
 $5 \rightarrow 2$   
 $6 \rightarrow 1$

95)

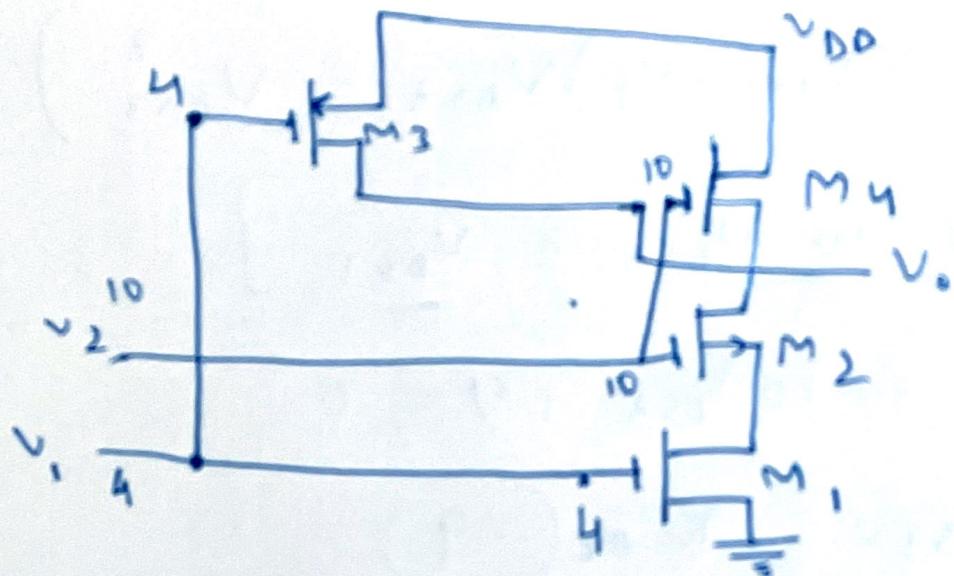

$$V_1 = 4V, V_2 = 10V, V_{DD} = 10V$$

$$K = 0.25 \text{ mA/V}^2$$

$$V_T(M_1, M_2) = 1V$$

$$V_T(M_3, M_4) = -1V$$

when  $M_4$  is off,

$$V_{AS4} = 0 > V_{T4}$$

$$V_{AS3} = -6V < +V_{T3}$$

$\therefore$  Assume  $M_1, M_2$  active &  $M_3$  ohmic

$$i_3 = i_2 = i_1$$

$$i_1 = K(V_{AS1} - V_T)^2 = \frac{(4-1)^2 K}{= 9K}$$

$$i_2 = K(V_{AS2} - V_T)^2 = (9 - V_{DS1})^2 K$$

$$i_1 = i_2 \Rightarrow 9 - V_{DS1} = 3$$

$$V_{DS1} = 6$$

$$i_3 = k \left[ 2(v_{as3} - v_T) v_{DS3} - v_{DS3}^2 \right]$$

$$= k \left[ -10 v_{DS3} - v_{DS3}^2 \right]$$

$$v_{DS3}^2 + 10v_{DS3} + 9 = 0$$

$$v_{DS3} = -1 \text{ or } -9$$

Rejected as  
for active  
region,

$$v_{DS} > v_{as} - v_T \\ = -5$$

$$\therefore v_{DS3} = -1$$


$$\therefore v_{DS3} \geq v_{as3} - v_T = -5V$$

$\therefore M_3$  in Ohmic region.

$$v_{DS2} = V_o - v_{DS1} = 3V \geq v_{DS2} - v_T = 3V$$

$$v_{DS1} = 6V \geq v_{as1} - v_T = 3V$$

Q6)

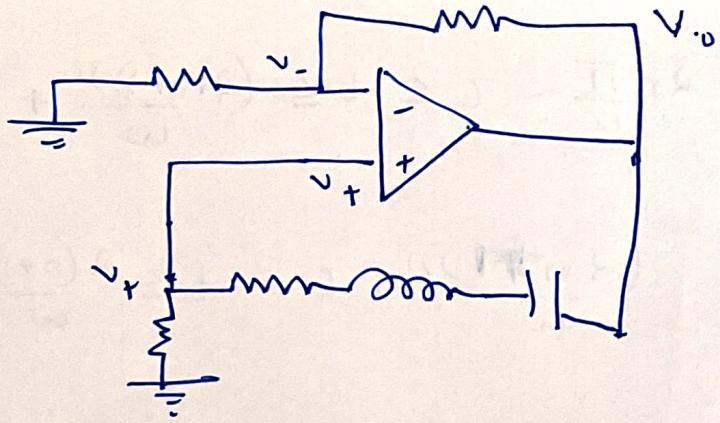

Assuming virtual short,  $v_+ = v_-$

$$\frac{v_o - v_-}{100} = \frac{v_-}{10}$$

$$v_o = 11 v_-$$

$$\frac{v_+}{R} = \frac{v_o - v_+}{|z|}$$

$$\frac{v}{R} = \frac{11 v_-}{|z|} \quad [v = v_- = v_+]$$

$$|z| = 10 R$$

$$100 R^2 = 5^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \times 10^{-6}$$

$$10 R > 5$$

$$\boxed{R > 0.5 \text{ k}\Omega}$$

$$\boxed{R > 500 \Omega}$$

$$\text{For } R = 500, \quad \omega = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{2 \times 10^{-9} \times 5 \times 10^{-6}}} = \boxed{10^6 \text{ rad/s}}$$